

TBA 435(A X5)	Z-IC	+8,5V, 0,1A	2a	7808/TO-220	17b	6
TBA 440 C	LIN-IC	. TV, Video-ZF, AGC (PNP-Tuner)	16-DIP	-		
TBA 440 N	LIN-IC	=TBA 440 C: AGC (NPN-Tuner)	16-DIP	-		
TBA 440 P	LIN-IC	=TBA 440 C	16-DIP	-		
TBA 440 Q	LIN-IC	=TBA 440 C: Fig. →	16-QIP	-		
TBA 450(N)(Q)	LIN-IC	Stereo-Decoder	16-DIP/QIP	-		**
TBA 460(Q)	LIN-IC	AM/FM-ZF + NF-V	16-DIP/QIP	-		**
TBA 480(Q)	LIN-IC	TV-Ton-ZF	16-DIP/QIP	-		**
TBA 490	LIN-IC	Stereo-Decoder	16-DIP	-		**
TBA 500 N,P(Q)	LIN-IC	CTV, Video, N:AGC=neg., P:AGC=pos.	16-DIP/QIP	-		**
TBA 510(Q)	LIN-IC	CTV, PAL Chroma-Signal	16-DIP/QIP	TBA 510	16-DIP/QIP	*
TBA 520(Q)	LIN-IC	CTV, PAL Synch.-Demodulator	16-DIP/QIP	TBA 520	16-DIP	*
TBA 530(Q)	LIN-IC	CTV, PAL RGB-Matrix	16-DIP/QIP	TBA 530	16-DIP	*
TBA 540(Q)	LIN-IC	CTV, PAL Referenz-Osc.	16-DIP/QIP	TBA 540	16-DIP	
TBA 550(Q)	LIN-IC	TV, Video Signal-Prozessor	16-DIP/QIP	-		**
TBA 560 A,B,C(Q)	LIN-IC	CTV, PAL Chroma-, Video-Signal	16-DIP/QIP	TBA 560 C	16-DIP	*
TBA 570(A,C)	LIN-IC	AM/FM-Empfänger/receiver	16-DIP	-		**
TBA 570(... )Q	LIN-IC	=TBA 570(A,C): Fig. →	16-QIP	-		**
TBA 625 A(X5)	Z-IC	+5V, 0,15A	2a	7805/TO-220	17b	6
TBA 625 B(X5)	Z-IC	+12V, 0,15A	2a	7812/TO-220	17b	6
TBA 625 C(X5)	Z-IC	+15V, 0,15A	2a	7815/TO-220	17b	6
TBA 641 A....	LIN-IC	NF-E, 12V, 2,2W(9V/4Ω)	14-QIP+c,d	-		**
TBA 641 B....	LIN-IC	=TBA 641A: 16V, 4,5W(14V/4Ω)	14-QIP+d,j	-		**
TBA 651	LIN-IC	AM-Tuner + ZF	16-QIP	-		**
TBA 700	LIN-IC	AM/FM-Empfänger/receiver	16-DIP	-		**
TBA 720(A)	LIN-IC	TV, HA-Synchr. + Osc.	16-DIP	-		**
TBA 720(A)Q	LIN-IC	=TBA 720(A): Fig. →	16-QIP	-		**
TBA 730(Q)	LIN-IC	TV, VA-Osc.	16-DIP/QIP	-		**
TBA 750 A,B,C	LIN-IC	FM-ZF, TV-Ton-ZF	16-DIP	-		**
TBA 750(... )Q	LIN-IC	=TBA 750(... ): Fig. ▶	16-QIP	-		**
TBA 760(Q)	LIN-IC	TV, VA-Synchr.	16-DIP/QIP	-		**
TBA 780 X2	LIN-IC	=TBA 780 X7: Fig. →	14-QIP	-		**
TBA 780 X7	LIN-IC	FM-ZF, TV-Ton-ZF	14-DIP	-		**
TBA 790....	LIN-IC	NF-E, 9....15V, 0,65....3,4W	14-QIP+....	-		**
TBA 790 LC	LIN-IC	=TBA 790 LB: 15V, 2,2W	14-QIP	-		**
TBA 800	LIN-IC	TV, VA/NF-E, 30V, 1,5A, 5W(24V/16Ω)	12-QIP+b	TBA 800	12-QIP+b	
TBA 800 A	LIN-IC	=TBA 800: Fig. →	12-QIP+a	TBA 800	12-QIP+b	
TBA 800 C	LIN-IC	=TBA 800	12-QIP+b	TBA 800	12-QIP+b	
TBA 810 ACB	LIN-IC	NF-E, 28V, 3A, 6W(14V/4Ω)	12-QIP+a	TBA 810 AT	12-QIP+a	
TBA 810 AP	LIN-IC	NF-E, 20V, 3A, 6W(14V/4Ω)	12-QIP+a	TBA 810 AT	12-QIP+a	
TBA 810 AS	LIN-IC	NF-E, 20V, 2,5A, 6W(14V/4Ω)	12-QIP+a	TBA 810 AS	12-QIP+a	
TBA 810 AT	LIN-IC	NF-E, 25V, 3A, 6W(14V/4Ω)	12-QIP+a	TBA 810 AT	12-QIP+a	
TBA 810 CB	LIN-IC	=TBA 810 ACB: Fig. ▶	12-QIP+b	TBA 810 AT	12-QIP+a	
TBA 810 P	LIN-IC	=TBA 810 AP: Fig. →	12-QIP+b	TBA 810 AT	12-QIP+a	
TBA 810 S	LIN-IC	=TBA 810 AS: Fig. →	12-QIP+b	TBA 810 S	12-QIP+b	
TBA 810 SH	LIN-IC	=TBA 810 AS: Fig. ▶	12-QIP+b	TBA 810 S	12-QIP+b	
TBA 810 T	LIN-IC	=TBA 810 AT: Fig. →	12-QIP+b	TBA 810 AT	12-QIP+a	
TBA 820	LIN-IC	NF-E, 16V, 1,5A, 2W(12V/8Ω)	14-QIP	TBA 820	14-QIP	
TBA 820 CM	LIN-IC	=TBA 820: Fig. ▶	TO-100	-		
TBA 820 M	LIN-IC	=TBA 820: Fig. →	8-DIP	TBA 820 M	8-DIP	
TBA 830 G,R	LIN-IC	Mikrofon-Verstärker/amplifier	5	-		**
TBA 890(Q)	LIN-IC	TV, VA-Synchr.	16-DIP/QIP	-		**
TBA 900(Q)	LIN-IC	TV, Video	16-DIP/QIP	-		**
TBA 920(S)	LIN-IC	TV, HA-Kombination	16-DIP	TBA 920 S	16-DIP	
TBA 920 Q,T	LIN-IC	=TBA 920(S): Fig. ▶	16-QIP	TBA 920 S	16-DIP	
TBA 940(A)	LIN-IC	TV, HA-Synchr. (f. Thyristor-E)	14-DIP	TBA 940 A	14-DIP	*